
ELEC 3300 Introduction to Embedded Systems

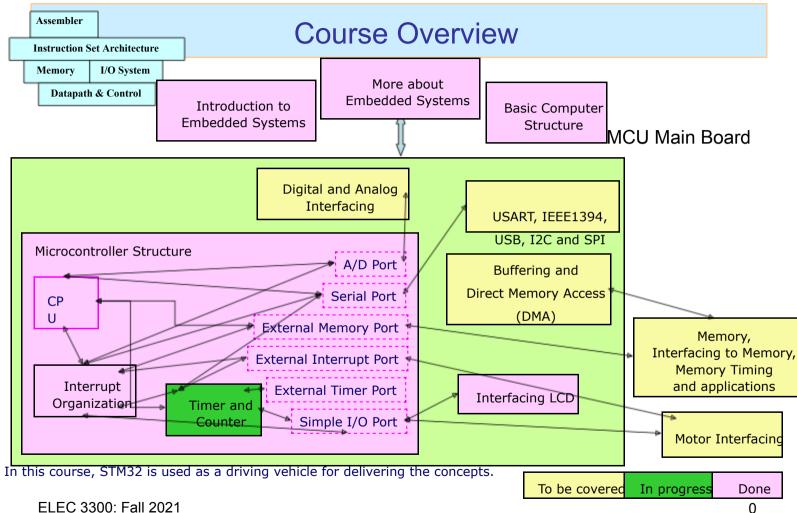Topic 7 Timer and Counter Prof. VINOD Prasad



Expected Outcomes

- On successful completion of this topic, you will be able to
- Summarize the importance of the timer in microprocessor
- Distinguish the features of timer and counter
- Demonstrate some applications of timers
- Understand the timing diagram of the general-purpose timers in STM32.

Why TIMERS?



CLOCK – display real time in multiple time zones


ALARM – alarm at certain (later) time(s)

STOPWATCH - measure elapsed time of an event

TIMER – count down time and notify when count becomes zero (introduce a delay, count an event)


Timer-mode and counter-mode operation

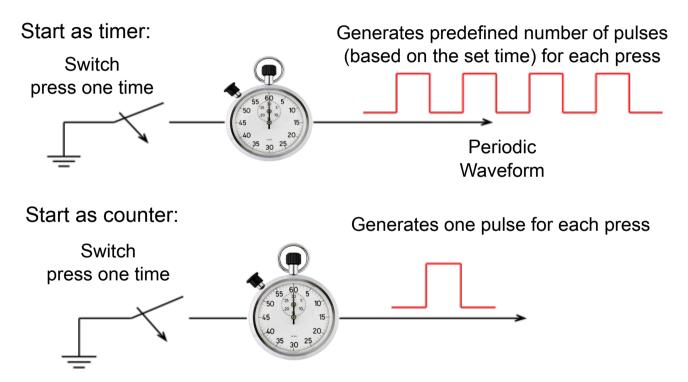Two modes of operation: TIMER and COUNTER modes



Timer-Mode Operation

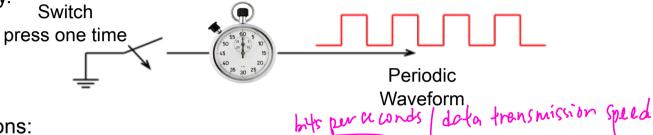 An output pulse generated each time the counter reaches zero (or preset value) provides a signal with a software-programmable frequency.



Applications:

A common use for this output is as a baud rate generator for a serial communication interface (different CLK frequencies for different baud rates). generating waveforms for audible tones.

(Try this https://www.szynalski.com/tone-generator/)
Timing the length of event

counter
reaches zero

the frequency is programmable by software.

OR

periodic interrupt signals

OR

periodic output pulses

ELEC 3300: Fall 2021


0

Counter-Mode Operation

 It is useful for interfacing to other devices that produce streams of possibly non-period pulses that must be counted °




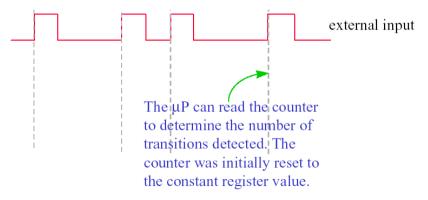- Applications:
- Count the number of times that a user has pressed a key.



Real-world Examples of Counter-mode operation

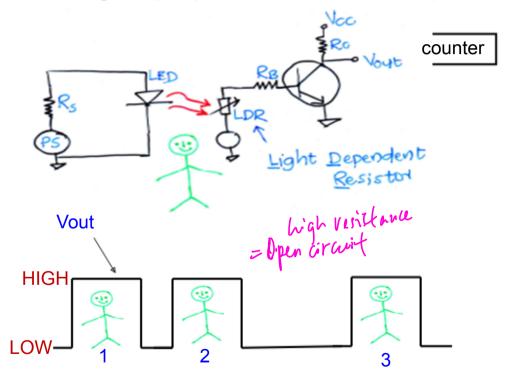Counting People (customers of 7-11 store)



Condition #1 - No person between LED and LDR:

LDR turns ON while receiving light from LED □ sufficient base current □ large collector current □ transistor ON (saturation) □ Vout is LOW.


Condition #2 - Person between LED and LDR:

LDR turns OFF as no light from LED □ No base current □ No collector current □ transistor OFF □ Vout is HIGH.

Counter value = number of pulses = number of people

Timer Structure

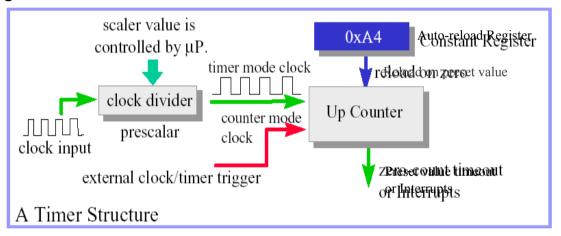- Devices that use a high speed clock input to provide a series of time or count related events
- Building block of a timer




- Other important registers:
- Counter Register, Mode Register, Control Register, Status Register

 Counter Register, Mode Register, Control Register, Status Register, Mode Register,

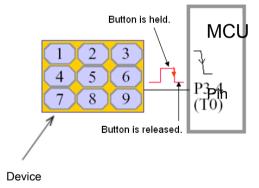Example 1 – Event Counting

- Say, you want a microprocessor to know how many times a user has pressed a key.
- We can connect the keypad to the microprocessor pin line, and then use Timer X to detect the key stroke which sends a pulse to pin.



Pseudo code:

Timer initialization Turn on Timer X

.

.

while (the button is pressed)

Event counting

Read counter register

Description

Abstract idea of project (Define the functionality of the system)

Data format / representation

Programming Language

Communication Protocol

Physical connection (Pins assignment)


Hardware devices (Microcontroller, Peripherals)

0


Step 1: Initialization
Configure the type of Timer / Counter

Step 2: Implementation Run / Stop the timer, Read the counter register


Example 1 – Event Counting

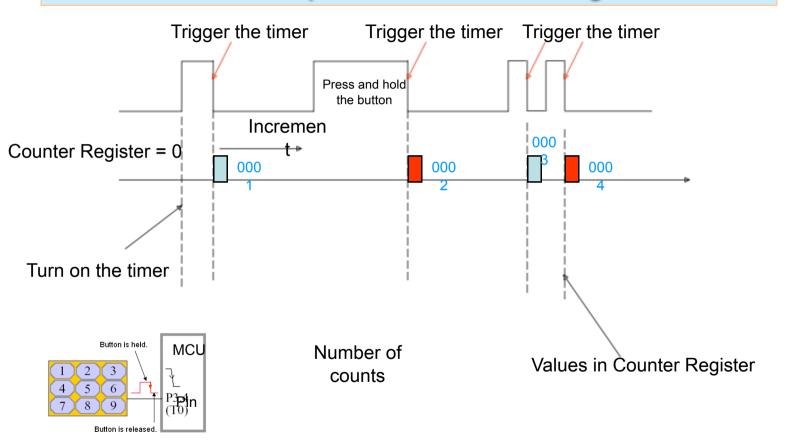

Example 1 – Event Counting using STM32

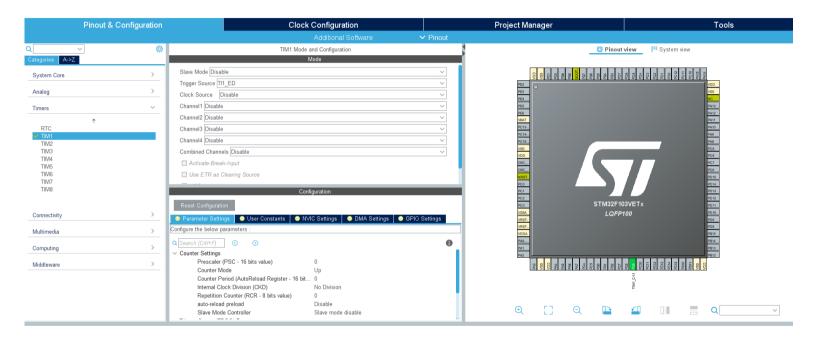

Example 1 – Event Counting using STM32

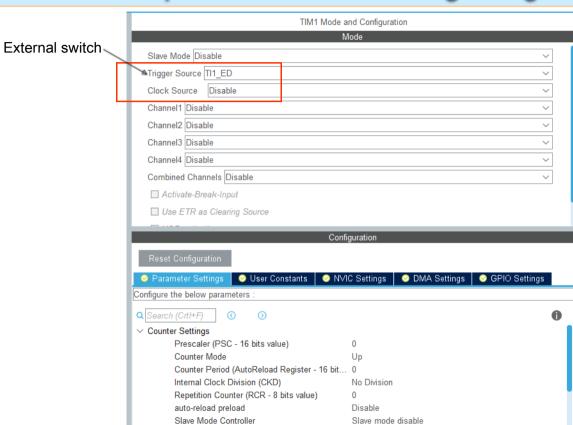

- To measure how long (time) a key is being pressed:
- We can connect the keypad to a another pin.
- In this way, the timer X will run when pulse is high (or a key is held down). When pulse is low (or a key is released), the timer X will be stopped.

Abstract idea of project (Define the functionality of the system)

Data format / representation

Programming Language

Communication Protocol

Physical connection (Pins assignment)

Hardware devices (Microcontroller, Peripherals)

1 2 3 4 5 6 7 8 9 P3.2 (Rino) Pseudo code:

Timer initialization Turn on Timer X Step 1: Initialization

Configure the type of Timer / Counter

.....


If the pulse is high, trigger the timer

If the pulse is low, stop the timer X


Step 2: Implementation Run / Stop the timer, Read the counter register

Read counter register

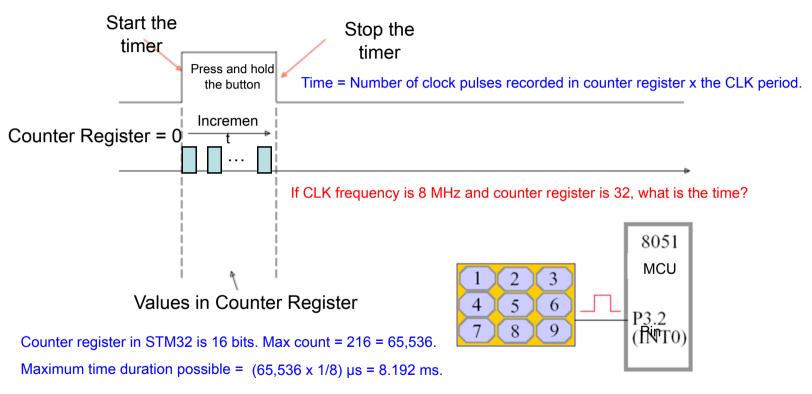• From the current counter value and the frequency of the input clock, we can calculate the time elapsed for the event.



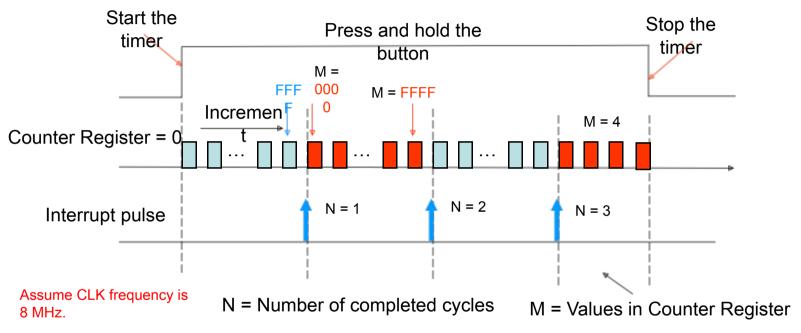
Assume that your application needs to time more than 8.192 ms. How will you achieve this?



Total number of count = $(N \times 216)+M$

Total time = $[(N \times 216) + M] / 8$

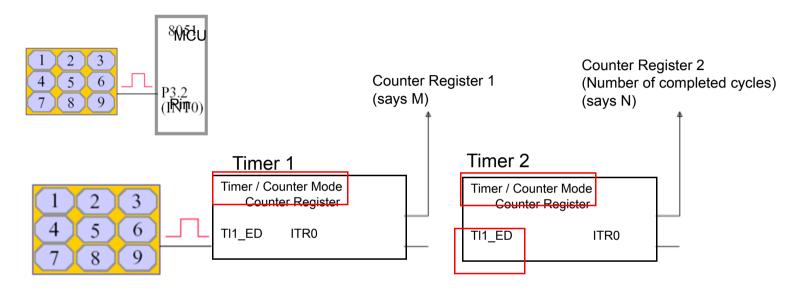
Design Problem: The application engineer tells you that the time needed for an event is at least 1 sec. How will you that the time needed for an event is at least 1 sec. How will you that the time needed for an event is at least 1 sec. How will you that the time needed for an event is



For every increment in 'N' (which happens when timer count hits FFFF), interrupt pulse will be generated at ITR0 of Timer 1, which triggers the input TI1_ED of Timer 2.


In-class Quiz (Question 1 – 4)

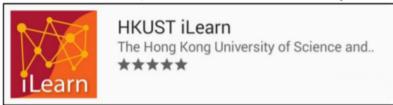
For Android devices, search HKUST iLearn at Play Store.



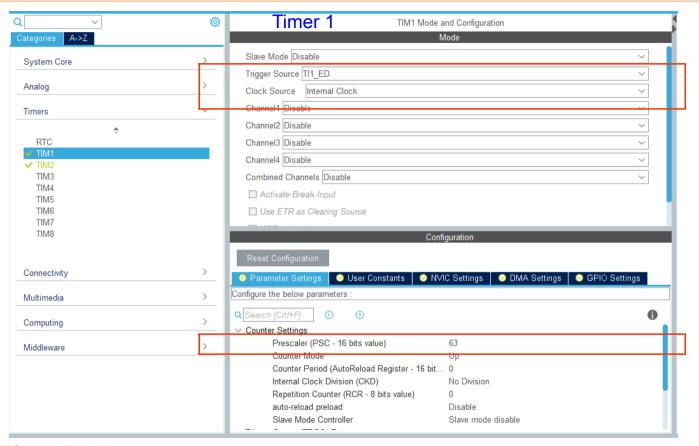
For iOS devices, search **HKUST iLearn** at App Store.





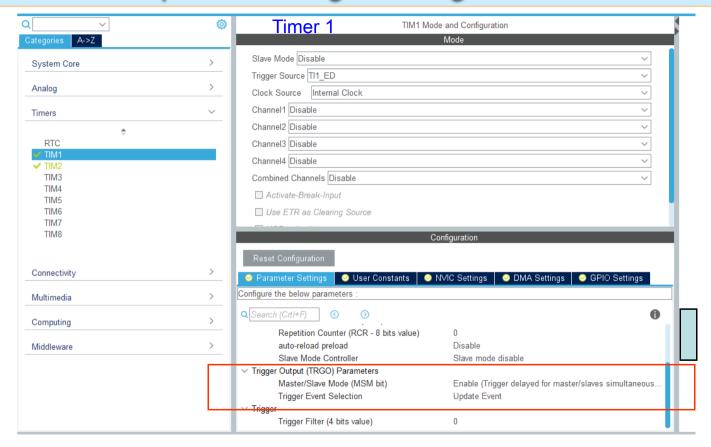


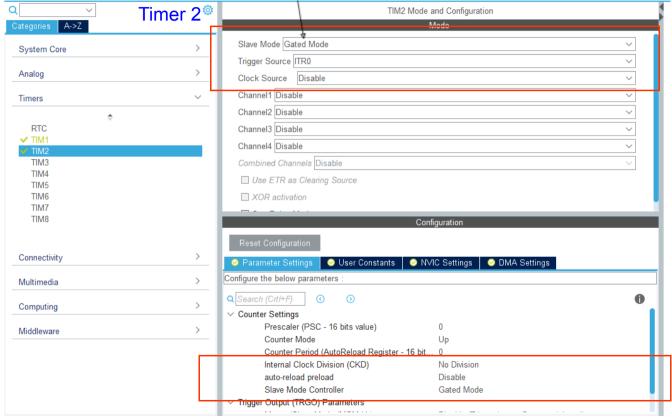Gated mode: counter Active only when the level of input signal is High.



Program flow

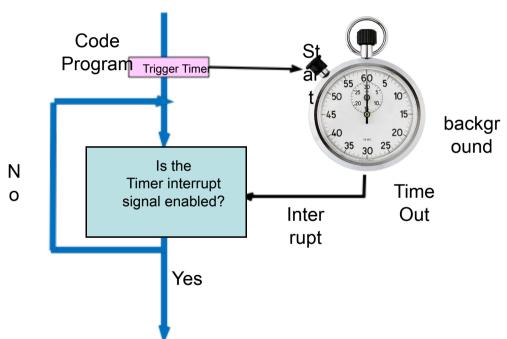
Timer can be used as a <u>delay function</u> call.



Main program is put under hold until the timer time out and trigger the interrupt, which will enable the main program to resume. Purpose - To introduce a delay to the main program.

Program flow

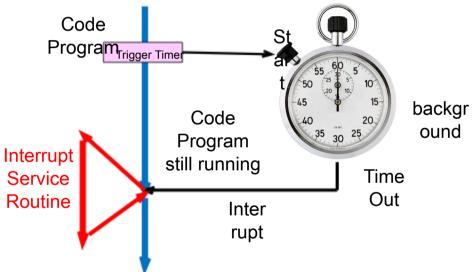Interrupt I/O allows the clock to interrupt the CPU announcing that the device requires attention. This allows CPU to ignore devices unless they request servicing via interrupt




Main program continues to run until the timer time out and triggers the <u>interrupt</u>. Upon receiving the interrupt signal, the main program will stop execution, branch to execute the ISR and return to resume the main program after completing the ISR.

- The high-density STM32F103xx performance line devices include up to two advanced control timers, up to four general-purpose timers, two basic timers, two watchdog timers and a SysTick timer.
 - TIM1 / TIM8 advanced control timers
 - TIM2 / TIM3 / TIM4 / TIM5 general purpose timers
 - TIM6 / TIM7 basic timers

Table 4 compares the features of the advanced-control, general-purpose and basic timers.

Table 4. Timer feature comparison


Timer	Counter resolution	Counter type	Prescaler factor	DMA request generation	Capture/compare channels	Complementary outputs
TIM1, TIM8	16-bit	Up, down, up/down	Any integer between 1 and 65536	Yes	4	Yes
TIM2, TIM3, TIM4, TIM5	16-bit	Up, down, up/down	Any integer between 1 and 65536	Yes	4	No
TIM6, TIM7	16-bit	Up	Any integer between 1 and 65536	Yes	0	No

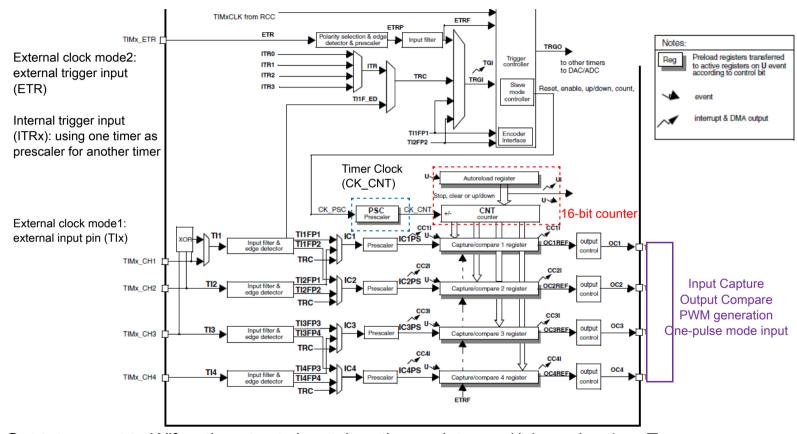

Oatptutecenveratre a Welfiers the wordern texture attaloas titure cognistere are ditstegeral war (eg. To interate to Datil A pergrices to elapsed).


Generate the Timer Clock


Figure 101. Counter timing diagram with prescaler division change from 1 to 2

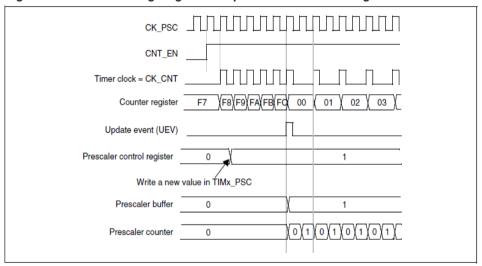



^{*} Upcounting configuration is employed.

With auto-reload features, says TIMx_ARR = 0X36h

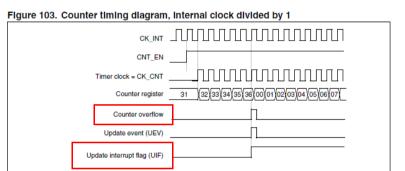

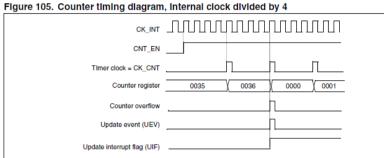

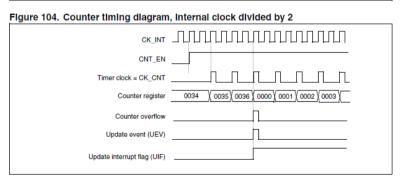


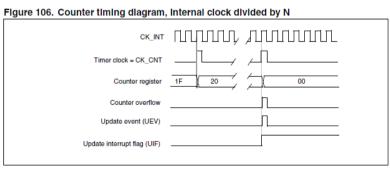

ELEC 3300 : Fall 20/21 Tim Woo 0

^{*} Upcounting configuration is employed.

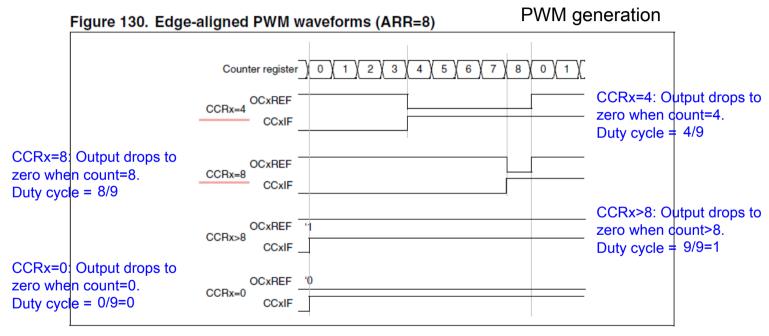ARR: Auto Reload Register. When ARR = 8, it will produce 0 - 8 counts (total 9 counts).



Resolution of duty cycle = 1/9.


How can we obtain a duty cycle of 50%? Solution: Set ARR = 9.

CCR – Capture Compare Register


^{*} Upcounting configuration is employed.

In-class Quiz (Question 5)

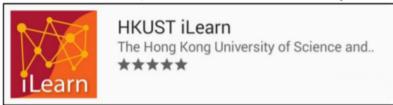For Android devices, search **HKUST iLearn** at Play Store.



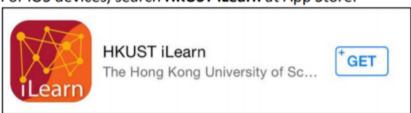For iOS devices, search **HKUST iLearn** at App Store.



If you are not using CubeMX:

In the initialization of timer, we need to configure

```
The parameters of input clock rate

TIMx Timebase includes

prescalar register (TIMx_PSC), auto-reload register (TIMx_ARR), etc

The parameters of output waveform

TIMx Output Compare, TIMx_CCRx Register
```

For the implementation stage, we just need to enable the timer / counter pin


The result will be stored in the Counter Register (TIMx_CNT), Output Compare Register (OCxREF), etc

Can you configure these settings in CubeMX?

Real-world Examples

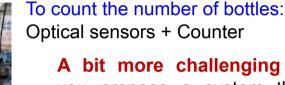Bottle counting (Mineral water bottling plant)





A bit more challenging problem: Can you propose a system that counts and displays the <u>number of customers in the 7-11 store at a given instance of time?</u>

Clue: You have to increase the count (when customer enters and decrease the count (when customer leaves).



Different problems, Similar solutions: Can you propose a system that counts and displays the <u>number of vacant seats in the upper deck</u> of KMB double decker bus?

Reflection (Self-evaluation)

- Do you ...
- List some applications for timer / counter operation ?
- State the important registers in the timer / counter operation?
- Write the sub-routines for event counting or timing the length of event?
- Describe the counter timing diagram in the count-down operation with different parameters (Clock frequency, up/down; auto-reload values)?

ELEC 3300: Fall 2021

0

